

## Sequential Machine Fundamentals

- 5-20.** Using timing diagrams analyze the operation of:  
 (a) The clocked RS Flip-Flop shown in Figure 5-22.  
 (b) The clocked D-Latch shown in Figure 5-23.
- 5-21.** Discuss why the avoidance of the indeterminability of a binary cell becomes increasingly important where clocked RS Flip-Flops are being used.
- 5-22.** By making a simple transformation, convert the RS Flip-Flop shown in Figure 5-22 to support the following schematic symbol (Figure P5-4).

 


Fig. P5-4.

- 5-23.** Using a timing diagram approach, analyze the T Flip-Flop shown in Figure 5-24. Include propagation delay in your analysis, illustrating the undesirable mode of operation (oscillation or hang) discussed in Section 5-15.
- 5-24.** Using the steps set forth in Section 5-17:  
 (a) Design a NAND cell centered LM Flip-Flop specified by the following characteristic table and schematic symbol (Figure P5-5).

$L$	$M$	$Q_n$	$Q_{n+1}$
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

 



Fig. P5-5.

- (b) Define the excitation table for the LM Flip-Flop.
- 5-25.** Using the steps set forth in Section 5-17:  
 (a) Define the characteristic table.  
 (b) Design a NAND cell-centered Flip-Flop.  
 (c) Define the excitation table for a SET dominant clocked SR Flip-Flop. This Flip-Flop is to always leave the basic cell in a SET condition if  $S$  and  $R$  are asserted together. Design in asynchronous SET and RESET functions.
- 5-26.** Repeat the steps specified in Problem 5-25 for the following design problem: Design a RESET dominant clocked RS Flip-Flop. This Flip-Flop is to always leave the basic cell in a RESET condition if  $S$  and  $R$  are ASSERTED together. Design in asynchronous SET and RESET functions.
- 5-27.** Repeat the steps specified in Problem 5-25 for the following design problem: Design a RS Flip-Flop that will leave the basic cell unchanged if the  $S$  and  $R$  are ASSERTED together.

**5-28.** Design a Flip-Flop specified by the following characteristic table. Check your circuit with Figure 5-25(b).

	$J$	$K$	$Q_n$	$Q_{n+1}$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

 **5-29.** Using all the information available, design a NOR cell centered POOPS-DINK ( $P, D$ ) Flip-Flop that operates as specified by the following table and schematic symbol (Figure P5-6):




$P$	$D$	Operation
0	0	Changes state with clock only if $Q = 1$
0	1	Changes state with clock only if $Q = 1$
1	0	Always sets the Flip-Flop with clock
1	1	Changes state with clock.

Fig. P5-6.

- Show general model of your Flip-Flop.
- Define the characteristic table.
- Define the excitation table.
- Show completely documented schematic diagram.

 **5-30.** Repeat Problem 5-29 for the SN Flip-Flop that is specified by the following table and schematic symbol (use NAND cell) (see Figure P5-7).



$S$	$N$	Operation
0	0	Changes state with clock only if $Q = 0$
0	1	Changes state with clock only if $Q = 1$
1	0	Always sets with clock
1	1	Remains unchanged

Fig. P5-7.

**5-31.** Is it possible to design a T Flip-Flop that triggers on the rising-edge of the clock and within reasonable limits avoid the oscillation or hang problems associated with T Flip-Flops? Outline your method of attack for solving the problem.

- 5-32.** Using the method outlined in Section 5-18, carry out the following conversions.
- (a) Convert a D-Latch to a JK.
  - (b) Convert a JK Flip-Flop to a D-Latch.
  - (c) Convert a JK Flip-Flop to a T.
  - (d) Convert a T Flip-Flop to a JK.
- 5-33.** Using the method outlined in Section 5-18, carry out the following conversions.
- (a) Convert a D Flip-Flop to the PD Flip-Flop specified in Problem 5-29.
  - (b) Convert a JK Flip-Flop to the SN Flip-Flop specified in Problem 5-30.
- 5-34.** In your own words discuss the “hows” and “whens” the 1’s and 0’s catching problem arises when using a MASTER/SLAVE Flip-Flop. How does the asynchronous input create a problem?
- 5-35.** Design, using the methods outlined, a D MASTER/SLAVE Flip-Flop.
- 5-36.** In your own words discuss the three types of JK Flip-Flops triggering discussed in Section 5-19. Draw comparisons between the three and list what you see as advantages and disadvantages of each.
- 5-37.** Draw a timing diagram and illustrate your understanding of SETUP and HOLDING time. Give a qualitative description of each and how these specifications relate to the hardware of the Flip-Flop.
- 5-38.** In your own words discuss clock skew. Discuss why clock skew can create data transmission problems.
- 5-39.** Consider you are far off in Futz-a-too and you have burned out your last J-K falling-edge trigger Flip-Flop which was used as a T Flip-Flop with T ASSERTED LOW. But all is not lost—you have one rising-edge triggered D Flip-Flop, and the following gates (not packages) on your board: one INVERTER, one two-input OR gate, and two two-input NAND gates.
- (a) Using these devices *design* (show all design work) a circuit which will replace your burned out T Flip-Flop. (i) Draw your conversion model. (ii) Draw your circuit.
  - (b) You are given the following propagation delay parameters:

Inverter—10 nsec  
 All two-input gates—20 nsec  
 D Flip-Flop  
     —set up time = 20 nsec  
     —hold time = 5 nsec

What is the set up and hold time for your new Flip-Flop?